

lec 24


Summary of Single Stage Amplifiers

Type	Small Signal Gain (Low freq.)	Bandwidth	R <sub>in</sub> (low freq.)	R <sub>out</sub> (low freq.)
<p><u>Common Source</u></p>	$-g_m (r_o \parallel R_D)$ <p>HIGH (Inverting)</p>	$\frac{1}{\{R_{in}(1+g_m R_D) C_{gd} + R_{in} C_{gs} + R_D C_{db} + R_D C_{db}\}}$ <p>LOW (Miller)</p>	$\infty$ <p>HIGH</p>	$r_o \parallel R_D$ <p>HIGH (for large gain <math>\times R_D</math>)</p>
<p><u>Common Drain</u> (Source Follower)</p>	$\frac{g_m (r_o \parallel R_S)}{1 + (g_m + g_{mb})(r_o \parallel R_S)}$ $\approx 1$ <p>(Non inverting)</p>	$\frac{1}{\{R_{in} C_{gd} + \frac{C_{gs} + C_{sb}}{g_m + g_{mb}}\}}$ <p>HIGH (No Miller)</p>	$\infty$ <p>HIGH</p>	$R_S \parallel r_m \parallel r_{mb} \parallel r_o$ $\approx R_S \parallel r_m$ <p>LOW</p>
<p><u>Common Gate</u></p>	<p>(Assuming <math>R_{in} \approx 0</math>)</p> $(g_m + g_{mb} + r_o^{-1})(r_o \parallel R_D)$ $\approx (g_m + g_{mb})(r_o \parallel R_D)$ $\frac{(g_m + g_{mb}) r_o R_D}{R_D + r_o + R_{in}(1 + (g_m + g_{mb}) r_o)}$ <p>HIGH (Noninverting)</p>	$\frac{1}{\{(C_{gs} + C_{sb})(R_{in} \parallel \frac{1}{g_m + g_{mb}}) + (C_{gd} + C_{db}) R_D\}}$ <p>HIGH (No Miller)</p>	<p>Assuming <math>R_{in} \approx 0</math></p> $r_m \parallel r_{mb} \parallel r_o$ $\approx r_m$ <p>LOW</p>	<p>Assuming <math>R_{in} \approx 0</math></p> $r_o \parallel R_D$ <p>HIGH</p>

# Multi-stage Amplifiers

## Impedance Viewpoint


### Voltage "Sensor"

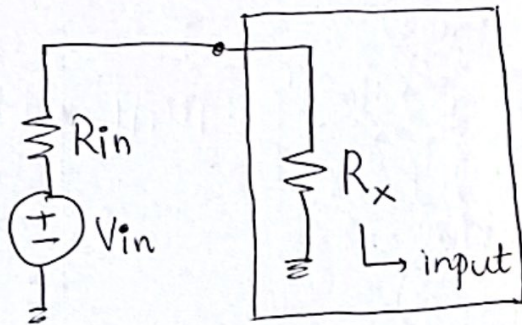

$R_x \rightarrow \infty \Rightarrow$  Good voltage sensor.  
Since  $V_{in}$  appears across it

$\hookrightarrow$  input impedance of voltage sensor.

### Current Sensor

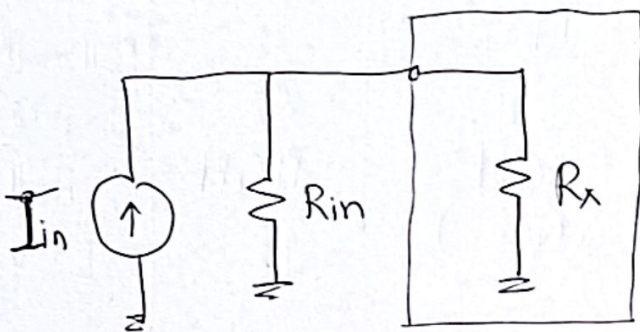


$R_x \rightarrow 0 \Rightarrow$  Good current sensor.

## Maximum Power Transfer

$> R_x = R_{in}$  (given  $R_{in}$ ).

$> \underline{\text{Note}}$ : Amplifier gain is a function of  $R_{load}$  too!


Voltage "drivers"

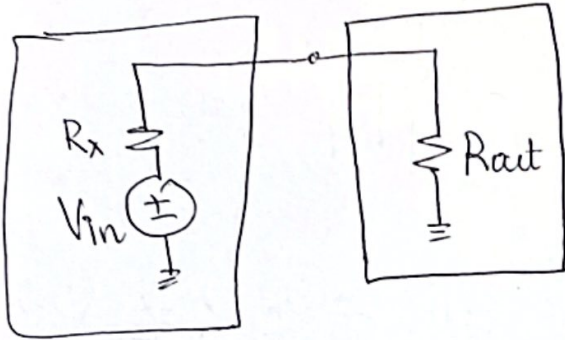

$R_x \rightarrow 0$

Note here  $V_{in}$  is given!

Current "drivers"

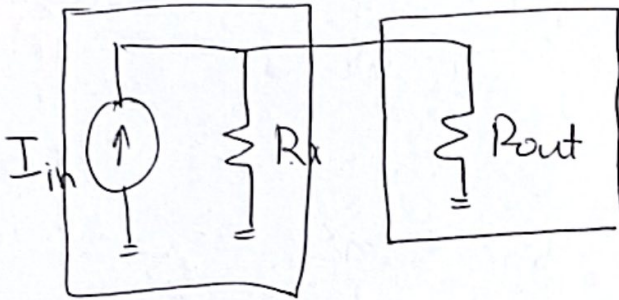


$R_x \rightarrow \infty$

Amplifier Type

Voltage Amp ( $V_{sense}$   $V_{drive}$ )

$R_{in} \rightarrow \infty$   
 $R_{out} \rightarrow 0$

(Common Gate)  
*Drain*

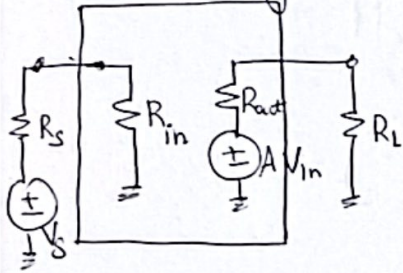


Current Amp ( $I_{sense}$   $I_{drive}$ )

$R_{out} \rightarrow \infty$

$R_{in} \rightarrow 0$


(Common Gate)

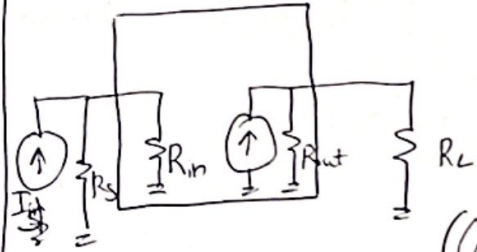

Transconductance Amp ( $V_{sense}$   $I_{drive}$ )


$R_{in} \rightarrow \infty$   
 $R_{out} \rightarrow \infty$

(Common Source)


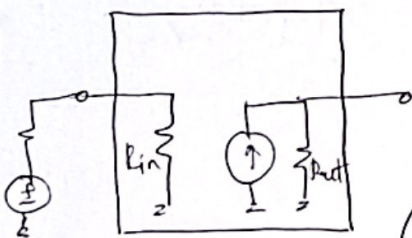


Transimpedance Amp ( $I_{sense}$   $V_{drive}$ ) (TIA)

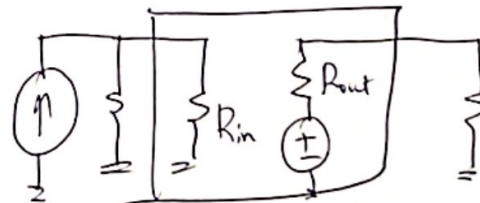$R_{in} \rightarrow 0$   
 $R_{out} \rightarrow 0$



# Design Example

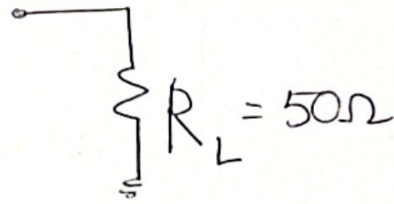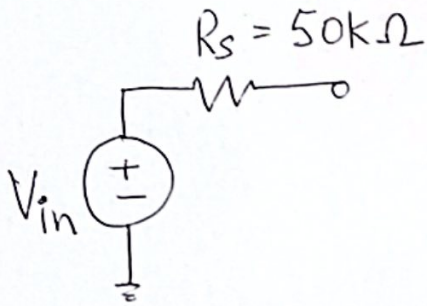

Specs:  $|A_v| = 100$

$f_{3dB} = ~~20MHz~~ 15MHz$

$V_{DD} = 1.8V$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

$$C_{gs} = W L_{ov} C_{ox} + \frac{2}{3} W L C_{ox}$$

$$C_{gd} = W L_{ov} C_{ox}$$

Parameters: at  $I_D = 200\mu A$ ;  $g_m = 5mS$

$r_o = 40k\Omega$

$C_{gs} = 100fF$

$C_{gd} = 20fF$

$C_{db} = C_{sb} = 30fF$

} NMOS.

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$W$  &  $I_D$  scaled by  $N \Rightarrow g_m \rightarrow N g_m$

Attempt (1) Common Source. (Ignoring  $R_L$ )

Let  $R_o = 5k\Omega$

$$\Rightarrow A_v = -g_m (R_o \parallel r_o) = -5mS (5k\Omega \parallel 40k\Omega) = -22$$


● Miller  $\tau_{gs} = \frac{R_s \cdot C_{in}}{(50k) (C_{gs} + (1 + g_m R_D) C_{gd})} \approx 28ns$

$\underbrace{100f}_{C_{gs}} + \underbrace{23}_{(1+g_m R_D)} \cdot \underbrace{20f}_{C_{gd}}$   
 $\underbrace{\hspace{10em}}_{560f}$

$f_{3dB} \approx \frac{1}{2\pi(\tau)} \approx 5.6MHz$

> We need more gain & more BW!  $\Rightarrow$  Cascode.

Attempt 2 Cascode (CS + CG)

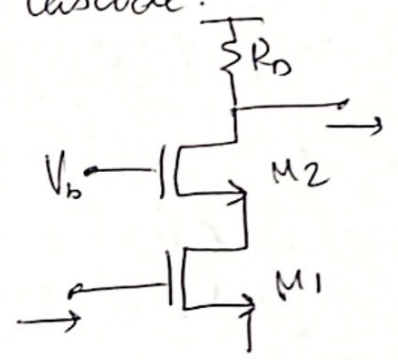

●  $A_v = -g_{m1} (R_D \parallel g_{m2} \underbrace{r_{o2} r_{o1}}_{5m \cdot 40k \cdot 40k})$

$\hat{=} -g_{m1} R_D$

$\hat{=} -25$

OCTC:  $\tau_{in} = R_s [C_{gs} + 2C_{gd}]$

$= 50k (100f + 40f) = 7ns$

$\tau_{mid}$  small since  $\frac{1}{g_m}$

$\tau_{out}$  small since  $(C_{db2} + C_{gd2})$  small &  $R_D$  is not too large.


●  $\Rightarrow f_{3dB} \approx \frac{1}{2\pi(7ns)} \approx 21.8MHz \rightarrow \text{Good!}$

> Connecting load  $50 \Omega$

$$\Rightarrow A_v = -g_{m1} (R_L \parallel R_o \parallel g_{m2} r_{o2} r_{o1})$$

$$= -5 \text{ mS} \cdot 50 = -0.25 \quad \text{!! BAD!}$$

Attempt 3 : Add CD buffer!

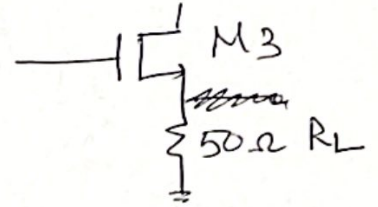

$$\text{CD gain} \approx \frac{g_{m3} R_L}{1 + g_{m3} R_L}$$

$$g_{m3} R_L = 5 \text{ mS} \times 50 = 0.25 \quad \Rightarrow \quad A_{v3} = \frac{0.25}{1.25} = 0.2$$

Increase  $g_{m3}$  to  $50 \text{ mS}$   $\Rightarrow I_{D3} = 2 \text{ mA}$


$$\Rightarrow N = 10$$

$$C_{gs3} = 1 \text{ pF}$$

$$C_{gd3} = 200 \text{ fF}$$

$$\Rightarrow A_{v3} = \frac{2.5}{3.5} \approx 0.7$$

$$\Rightarrow A_v = (-25)(0.7) = -17.8$$

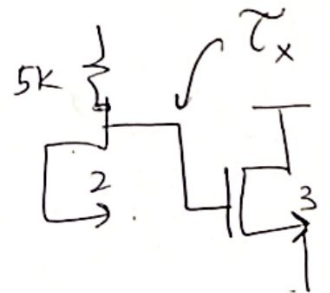

OCTC

$$\tau_x = 5 \text{ k} \left\{ \begin{array}{l} C_{gs3} \\ 1000 \text{ f} \\ \times 0.3 \\ + 200 \text{ f} \end{array} \right\} \approx \cancel{3.5 \text{ ns}} \quad \begin{array}{l} 2.68 \text{ ns} \\ 3.85 \text{ ns} \end{array}$$


Problem

$$\tau_{\text{total}} = \tau_{\text{in}} + \frac{3.85}{2.68} = 12.5 \text{ ns} \quad \begin{array}{l} 9.68 \text{ ns} \\ 10.5 \text{ ns} \end{array}$$

$$\Rightarrow f_{3\text{dB}} = \cancel{12.7 \text{ MHz}} \quad \begin{array}{l} 12.6 \text{ MHz} \\ 16.4 \text{ MHz} \end{array}$$

Attempt 4 : Isolate  $R_s$  from  $C_{gs1} + 2C_{gd1}$

Add Common Drain Buffer.

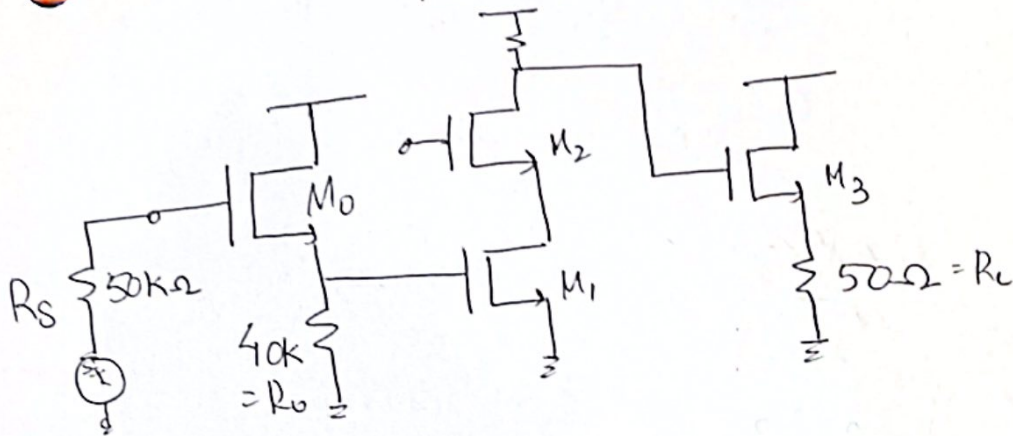

$$A_o = \frac{g_{m0} R_o}{1 + g_{m0} R_o} = \frac{(5m)(40k)}{1 + 5m \cdot 40k} = \frac{200}{201} \approx 1$$

OCTC

$$\tau_{in} = \underbrace{R_s}_{(50k)} \underbrace{C_{gd}}_{20 \text{ fF}} = 1 \text{ ns}$$

What about  $C_{gs}$ ? → Bootstrapped since  $V_{gs}$  is 0  
 Given that source follows gate.

$$\text{Miller point of view} \Rightarrow C_{gs}(1 - A_v) = C_{gs}(1 + 1) = 0$$

$$\Rightarrow \tau_{total} \approx 1 \text{ ns} + \cancel{2.85 \text{ ns}} 2.68 \text{ ns} \\ = \cancel{2.2 \text{ ns}} 3.68 \text{ ns}$$

$$f_{3dB} = \underline{\underline{43.2 \text{ MHz}}}$$

$$\text{Gain} = (0.995) (-25) (0.714) = -17.7$$

↑  
Bottleneck!

### Cascode with PMOS load


$$A_v = -g_{m1} (r_{o1} \parallel g_{m2} r_{o2} r_{o1}) \approx -g_{m1} r_{o1}$$

$$= 5\text{m} \cdot 40\text{k} = -200$$

$$\Rightarrow A_{v\text{total}} = -\underline{\underline{142}}$$

$$\frac{\text{BW}}{f_{3dB}} = \tau_{\text{mid}} \uparrow \text{ by } \times 8$$

$$f_{3dB} = 7\text{MHz}$$

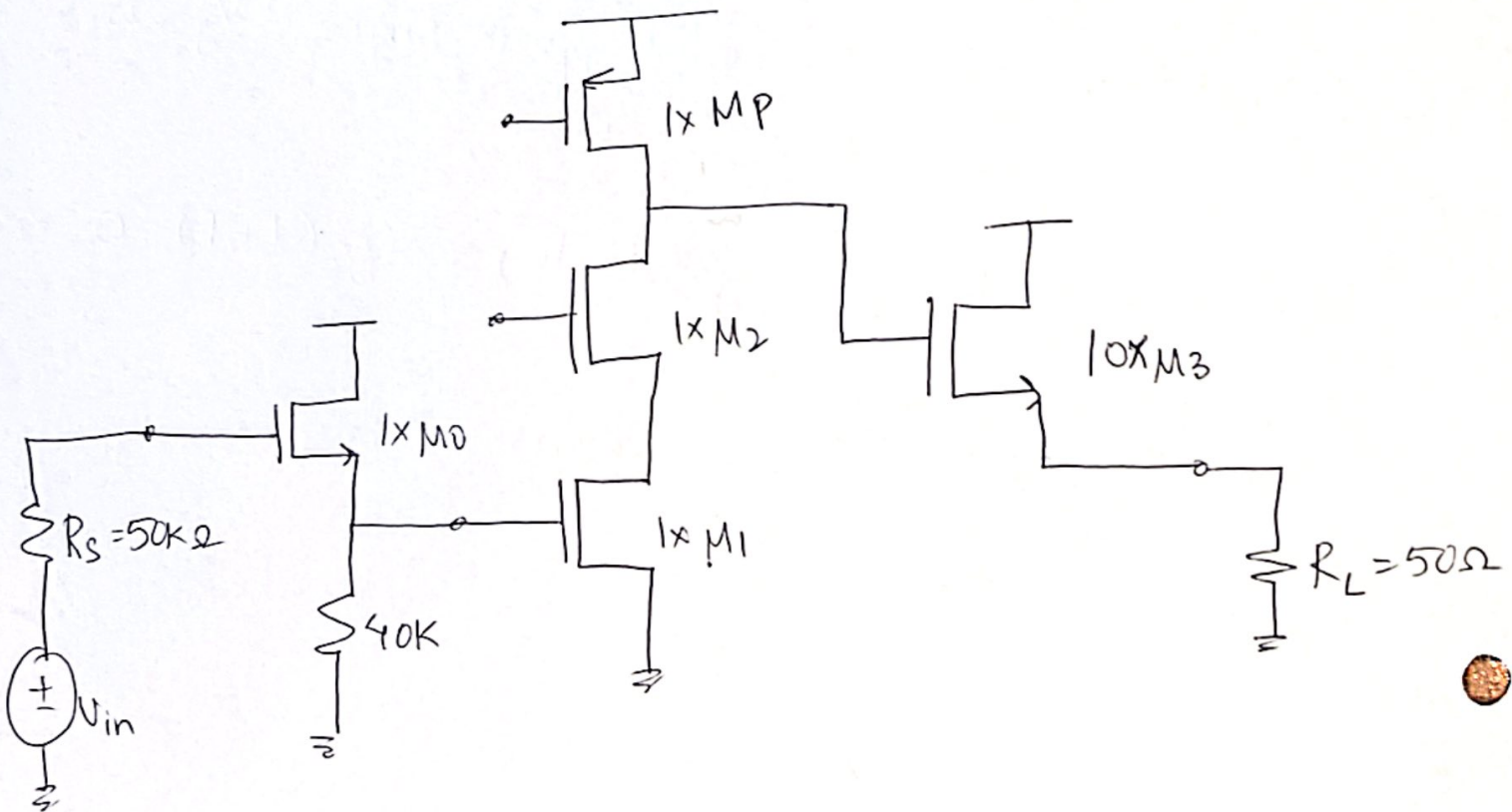

Re designing M3

$$\tau_x = 40k (100f \times 0.3 + 20f)$$

$$= 2.8n$$

$$\Rightarrow f_{3dB} = 53 \text{ MHz}$$

$$\frac{g_{m3} R_L}{1 + g_{m3} R_L} = \frac{1}{2} \Rightarrow g_{m3} = 20mS$$

$$\Rightarrow \boxed{N=4}$$

$$\Rightarrow A_v = -200 \times \frac{1}{2} = -100$$

$$\Rightarrow \tau = 40k (400f \times 0.3 + 80f)$$

$$= 40k (200f)$$

$$= 8nS$$

$$\tau = 8nS + 1nS = 9nS$$

$$\Rightarrow f_{3dB} = 17.68 \text{ MHz}$$